

AC Rectifier Bulk Capacitor Selection with Analysis + SPICE

By Ed Walker, President, Design/Analysis Consultants Inc., Tampa, Fla., and Christophe Basso, Application Manager, ON Semiconductor, Toulouse, France

This exercise demonstrates how the blend of analysis + simulation/testing can lead to a better understanding of circuit performance, compared to using analysis or simulation/testing alone.



Although SPICE can be a powerful tool, there are pitfalls in relying solely on simulation. To avoid unpleasant surprises, it's imperative that a SPICE simulation be anchored to a detailed understanding of the circuit.

Ideally, this includes a thorough analysis, capped off by testing.

A previous article in *Power Electronics Technology* by Christophe Basso¹ explained how, starting with a desired capacitor ripple voltage and defined load power, you can use SPICE to select the optimized value of the input rectifier circuit's filter capacitor. However, Ed Walker of Design/Analysis Consultants Inc. noted that this argument is not completely sound, and the defined SPICE approach may actually result in capacitor degradation or even explosion. That's because the selection of bulk capacitance is primarily determined by the *RMS ripple current rating* of the capacitor, not the ripple voltage. When ripple current is considered, the required capacitance typically will be much larger than when selection is based only on ripple voltage.

Creative Conflict

Although the previous article was intended to demonstrate the flexibility of SPICE for a common practical application, it should have included a discussion of the importance of capacitor ripple current. Thus, simply simulating a design without knowing the equations behind the circuit would inevitably lead to a poor-performing, unreliable device.

When the SPICE results of an ac rectification circuit with low source impedance were reviewed, we found that the charging current had a sawtooth shape, rather than the rect-

angular pulse that is often assumed. Was the conventional analysis assumption incorrect? Or was the sawtooth in Basso's example an unusual case, with the more typical waveform being rectangular?

Using the prior body of applications data (e.g., *Line Input AC-DC Conversion and Input Filter Capacitor Selection*, Unitrode Power Supply Design Seminar, 1986),

plus having performed confirming thermal measurements, the rectangular pulse waveform seemed like a good assumption. But as the SPICE simulation shows, it

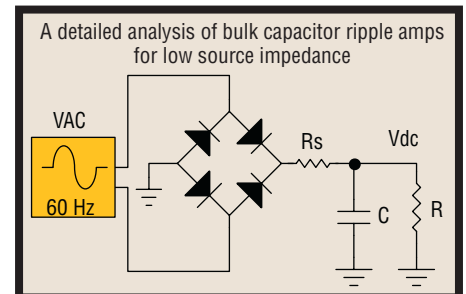


Fig. 1. A detailed analysis of bulk capacitor ripple Amps for low source impedance.

When ripple current is considered, the required capacitance typically will be much larger than when selection is based only on ripple voltage.

appears a sawtooth waveform will occur, at least for some circuit conditions.

Such conflict between analysis and simulation/test results is a typical and highly beneficial result of a thorough *worst-case analysis* design process, prodding the designer/analyst to resolve such discrepancies. In this case, the need for further analysis led us back to the past.

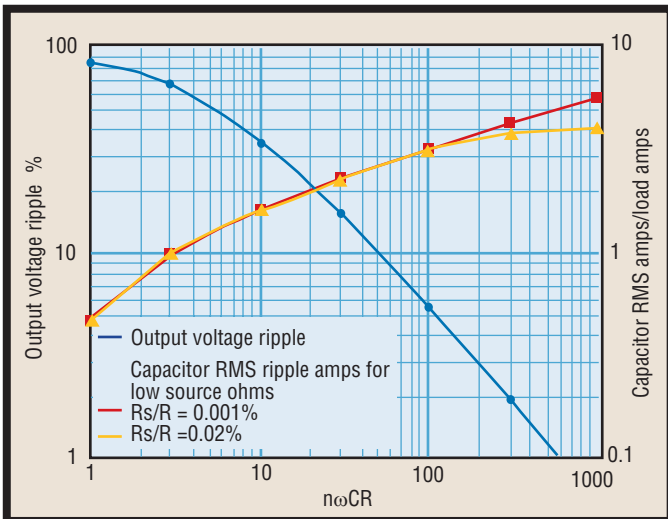


Fig. 2. Output voltage ripple and capacitor RMS ripple amps for low source impedance.

Augmenting Schade's Curves Using Analysis

The basic characteristics of rectifier circuits were determined by O.H. Schade back in 1943, as documented in his classic article, *Analysis of Rectifier Operation* (Proc. IRE, Vol. 31, No. 7, July 1943). "Schade's Curves," as they are known, present a wide range of rectifier performance in graphical form, including the effects of source impedance down to

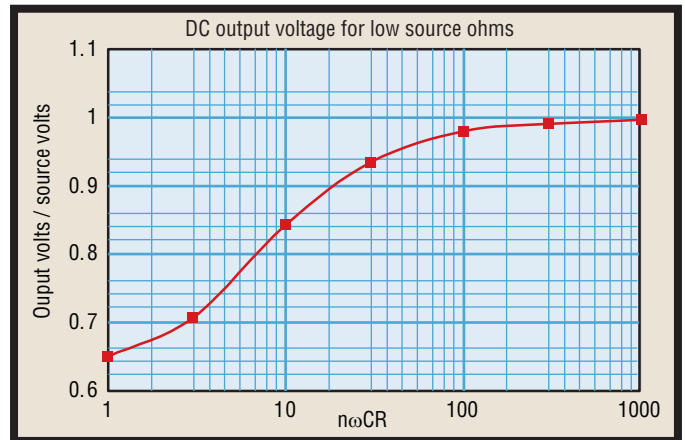


Fig. 3. DC output voltage for low source impedance.

0.02% of load impedance. However, Schade did not include curves of bulk capacitor ripple current. Therefore Walker performed an analysis of the bridge rectifier circuit to determine its capacitor RMS ripple amps for $R_s/R = 0.02\%$, and also for $R_s/R = 0.001\%$, since some modern designs may have extremely low source impedance. For circuit design purposes, output voltage and ripple were also computed. The analysis was performed using the *Design Master™* analysis software (Professional Edition). Results are presented in graphical form in Figs. 2 and 3.

High Voltage Ceramic Disk Capacitors


■ SUPER-FAST DELIVERY
■ CUSTOM VALUES

CKE is a quality manufacturer of competitively priced high voltage ceramic disk capacitors. We specialize in custom ceramic capacitors made to your specifications.



CKE

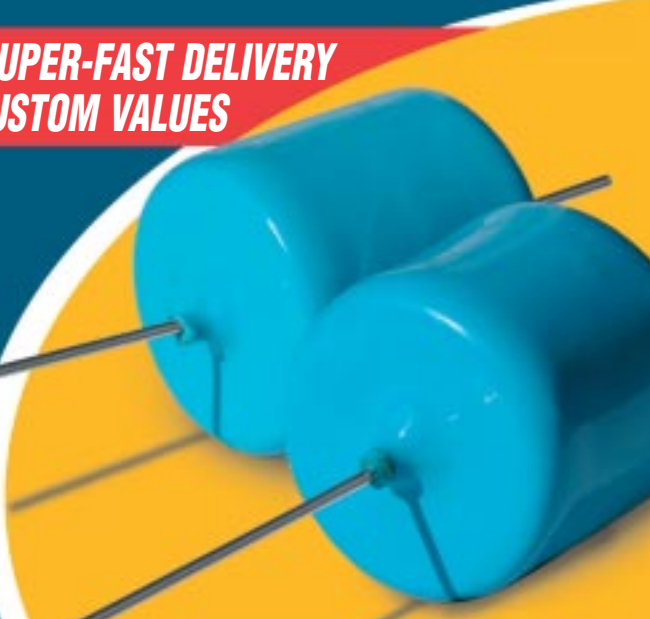P.O. Box 211 ■ Lucernemines, PA 15754
(724) 479-3533 ■ (724) 479-3537 FAX
e-mail: info@cke.com



■ Voltages up to 60kV
■ Wide range of temperature coefficients
■ Capacitance up to 15,000 pF

www.highvoltagecapacitors.com

CIRCLE 251 on Reader Service Card or freeproductinfo.net/pet

nωCR	Rs/R	Output Vpk-pk as % of VACpk		ICrms/Idc	
		Analysis	SPICE	Analysis	SPICE
10	0.001%	35.1	34.84	1.64	1.65
100	0.001%	5.4	5.34	3.25	3.31
1000	0.001%	0.6	0.58	5.77	5.85
10	0.02%	35.1	34.8	1.64	1.65
100	0.02%	5.3	5.32	3.21	3.23
1000	0.02%	0.6	0.57	4.24	4.24

Fig. 4. Comparing with SPICE. As can be seen, SPICE results are close to analytic calculations.

To see if you're using a properly rated bulk capacitor, simply measure your rectifier circuit's maximum ripple (e.g., at minimum load impedance and maximum Vac). Using the top graph, locate the percent ripple value on the left Y-axis and find the intersection with the ripple curve. Move up or down vertically and locate the intersection with the RMS amps curves, using the higher curve (lowest Rs/R) as applicable to your design. Now, move horizontally to find the rms factor on the right Y-axis. Multiply the factor times your max load amps. The result is the RMS ripple

amps rating that you should have used for the bulk capacitor, based on input considerations. You'll also have to add any contribution due to RMS load amps:

$$IC_{RMS}(total) = \text{SQR}(IC_{RMS}(input)^2 + IC_{RMS}(load)^2)$$

Example: Max ripple is measured to be ~ 5.5%. This intersects the ripple curve at nωCR = 100. Moving up vertically, the RMS intersection occurs at ~ 3.3. Assume that you have a max load current of 5 A. Therefore, the bulk capacitor should have a ripple amps rating of $5 \times 3.3 = 16.5A_{RMS}$. Add RMS load amps, if any, as described above.

New Designs

1. Select nωCR for the desired maximum output percent ripple. For example, for max peak-peak ripple = 10% of peak ac voltage, the ripple point occurs for nωCR ~ 50.

2. From nωCR, solve for the required bulk capacitor, using the *minimum* value of load resistance R. For example, if the load resistance is 100 V and the ac frequency is 60 Hz, then:

$$C = 50 / (n\omega R) = 50 / (2 * 2 * \text{Pi} * 60 * 100) = 663 \mu\text{F}$$

How to Use the Graphs

nωCR is given by

n = 2 for full wave bridge

$\omega = 2 \times \text{Pi} \times f$, where f = ac source frequency, Hz

C = bulk capacitance, farads

R = load ohms

Rs = total effective source impedance in ohms

RAPID PCB PROTOTYPING



Make Prototype Boards Yourself

Why waste valuable engineering time waiting for externally made PCB Prototypes? **Take back control** with rapid PCB prototyping equipment from LPKF. Clean, precise, easy-to-use and most importantly, **fast**.

- Circuit Board Plotter
- Through Hole Plating
- Multilayer Equipment
- SMT Assembly

For More Information on Rapid Prototyping Call **1-800-345-LPKF**

LPKF®
Laser & Electronics

North America: U.S.A. 503.454.4200 · fax 503.682.7151
 Germany: +49-51 31-70 95-0
 France: +33-1-60 86 16 23
 UK & Ireland: +44-1344-455046
 Japan: +81-3465-7105
 Australia & New Zealand: +61-2 9654-1873

Check LPKF web site for more locations and "Instant Contact"
www.lpkfusa.com
info@lpkfusa.com

Do it now!
Request LPKF's FREE Action Demo CD!

HERING Advertising · Germany © 2002, LPKF Laser & Electronics. All rights reserved.

CIRCLE 242 on Reader Service Card or freeproductinfo.net/pet

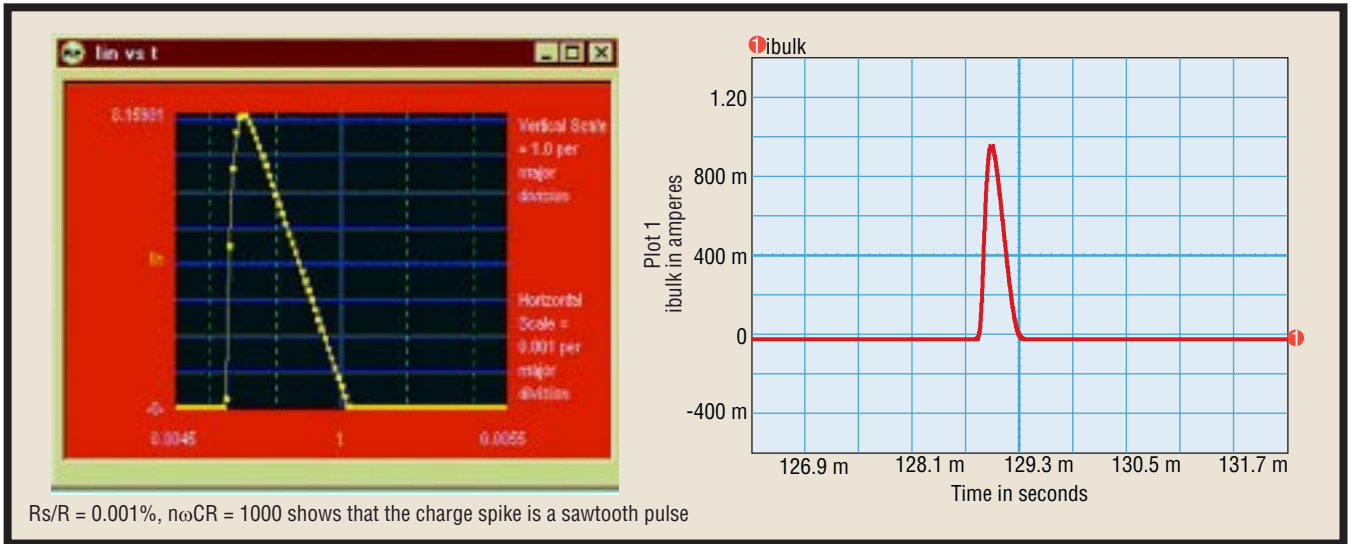


Fig. 5. For low-source impedances ($R_s/R = 0.001\%$) and with a high value of bulk capacitance ($n\omega CR = 1000$), the charge pulse is a sawtooth (analysis left, SPICE right).

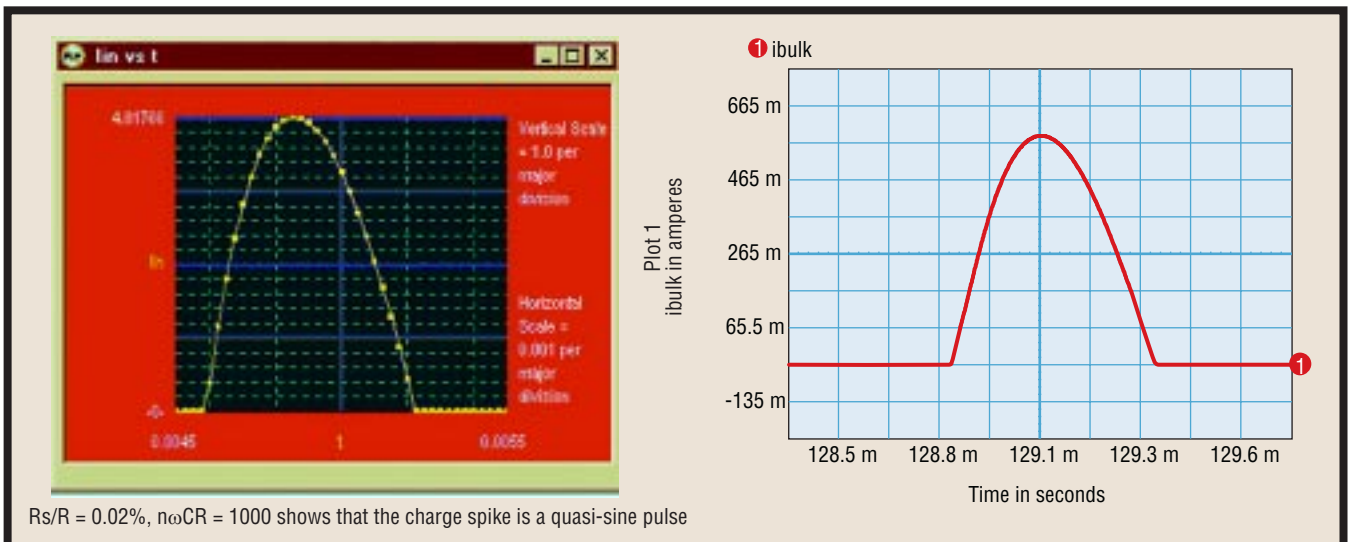


Fig. 6. For somewhat higher-source impedances ($R_s/R = 0.02\%$) and with the same high value of bulk capacitance ($n\omega CR = 1000$), the charge pulse becomes a quasi-sine shape.

3. Select a standard value of C and recompute $n\omega CR$. Let's assume a $680\text{-}\mu\text{F}$ capacitor was selected. From the capacitor RMS amps graph, maximum ripple amps occurs for maximum C , so use the maximum tolerance for the capacitor. Assuming 20%,

$$n\omega CR = 2 * 2 * \pi * 60 * (680E-6 * 1.2) * 100 \sim 62$$

4. Find the point where the new value of $n\omega CR$ intersects RMS amps line to determine the bulk capacitance ripple amps factor. In this example, the lines for $R_s/R = 0.001\%$ and 0.02% overlap, and the RMS value is

$$I_{C_{RMS}}/I_{dc} \text{ for } n\omega CR = 62 \text{ is } \sim 2.9 \text{ A per output dc amp}$$

5. Using the Dc Output Voltage graph, find the intersection of the curve at $n\omega CR$. For $n\omega CR = 62$, the intersec-

tion is at ~ 0.97 . Therefore, V_{dc} will be 97% of the AC source peak, less rectifier drop V_f . The worst case will be for maximum V_{ac} and minimum V_f . Assuming $V_{ac} = 120 \text{ Vac max} = 132 \text{ Vac}$ and $V_f \text{ min} = 1V \times 2$, then

$$V_{dc} = 0.97 * (1.414 * V_{acmax} - V_{fmin}) = 0.97 * (1.414 * 132 - 2) = 179 \text{ V}$$

6. Divide V_{dc} by the minimum load ohms to get the load amps:

$$I_{dc} = V_{dc}/R_{min} = 179/100 = 1.79 \text{ A}$$

7. Multiply I_{dc} times the ripple amp factor from Step 4 to get the required RMS ripple amps rating for the bulk capacitor:

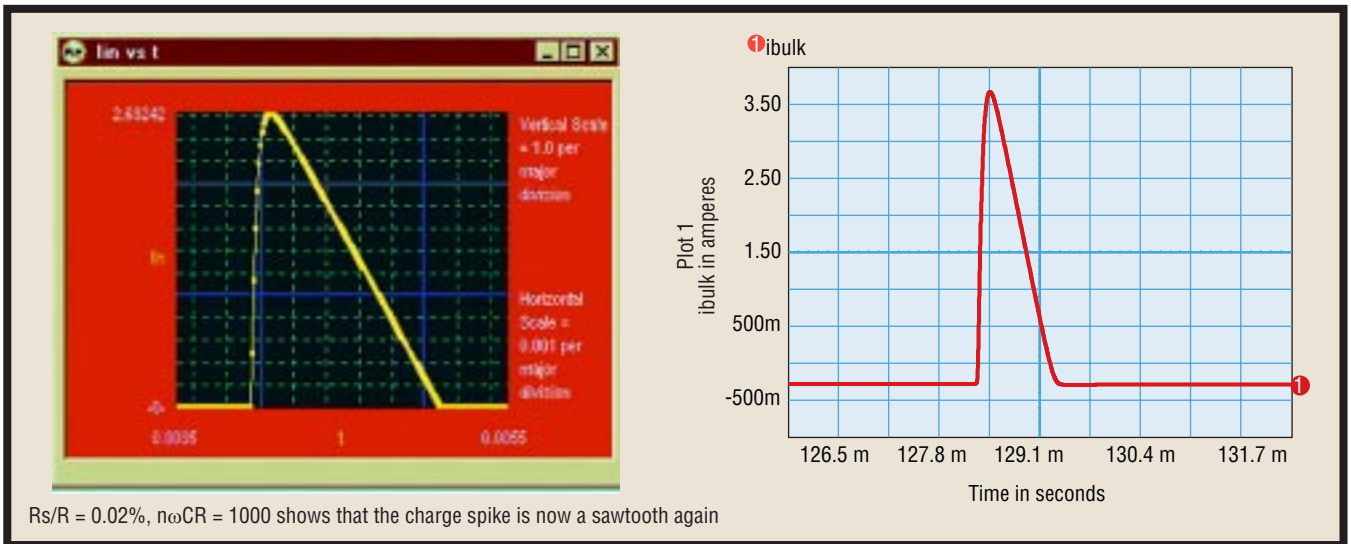


Fig. 7. As the capacitance decreases, the charge pulse again becomes a sawtooth.

$$I_{C_{RMS}} = I_{dc} * I_{C_{RMS}} / I_{dc} = 1.79 * 2.9 = 5.2 A_{RMS}$$

Note: If you can't find a capacitor with the desired ripple amps and want to select a larger capacitor with a higher ripple rating, you'll need to recompute using the new C value for $n\omega CR$, because as C increases, $I_{C_{RMS}}$ also increases.

8. After using the curves to find the value of RMS ripple due to the ac input charging current, don't forget to include the effects of any load-generated ripple current; e.g. switchmode power supply. The total capacitor RMS ripple amps requirement will be:

$$I_{C_{RMS}}(total) = \sqrt{I_{C_{RMS}}(input)^2 + I_{C_{RMS}}(load)^2}$$

Results Review

It's interesting to observe that a rectangular charging pulse doesn't really occur. For low source impedances ($R_s/R = 0.001\%$) and with a high value of bulk capacitance ($n\omega CR = 1000$), the charge pulse is a sawtooth, as shown in Fig. 5 (analysis left, SPICE right).

However, for somewhat higher source impedances ($R_s/R = 0.02\%$) and with the same high value of bulk capacitance ($n\omega CR = 1000$), the charge pulse becomes a quasi-sine shape, as shown in Fig. 6.

As the capacitance decreases, the charge pulse again becomes a sawtooth (Fig. 7).

As you move to low values of bulk capacitance, the charge pulse evolves into a duty-cycle sliced sinewave. However, because of high-output ripple voltage, this area of operation is generally of no interest for bridge rectifier design.

If you've been using the rectangular pulse waveform assumption for low source impedance cases, you've been pretty accurate. A sampling of cases using the rectangular waveform formula for $n\omega CR = 10, 100, \text{ and } 1000$ and $R_s/R = 0.02\%$ and 0.001% indicates a maximum $I_{C_{RMS}}$ error of ~24% too high to ~11% too low.

The actual value of source impedance will be distrib-

uted, consisting of ac supply ohms (e.g. transformer impedance), rectifier dynamic ohms, wiring and PWB path ohms, plus the effective ohms of any parasitic inductance. If you have source impedance R_s of ~0.01 Ω and a load R of 300 Ω , then $R_s/R = 0.0033\%$; use the 0.001% line. If you have source impedance R_s of ~0.1 Ω and a load R of 100 Ω , then $R_s/R = 0.1\%$; use the 0.02% line. If R_s/R is greater than 0.02%, your design will be safe but maybe not cost-optimized, since you may be over-rating your capacitor.

Analysis of the ratio of source-to-load ohms from 0.001% up to 100% can be obtained by using the Design Master *Bridge Rectifier Analysis* file; available free when you subscribe to *Design Master*™ Professional Edition. In addition to capacitor ripple current, the file also analyzes rectifier and transformer average, rms, and peak currents, average output voltage, and output ripple.

A SPICE simulation of a full-wave bridge rectifier circuit determined that the bulk capacitance charge current was a sawtooth waveform. This didn't match the assumption of a rectangular charge pulse, which is often used for rectifier analysis. A detailed analysis determined that the charging waveform could vary considerably, depending on circuit values. The analysis data were used to create graphs that allow the power supply designer to determine the appropriate value of bulk capacitor for a desired ripple voltage, and to also obtain the capacitor's required RMS ripple amps rating. The results of SPICE simulations closely matched the results of the detailed analysis. PETech

References:

1. "Sugar and SPICE: Determining Input Bulk Capacitor for Switchmode Power Supplies," *Christophe Basso, January 2002, Power Electronics Technology.*

For more information on this article, CIRCLE 342 on Reader Service Card